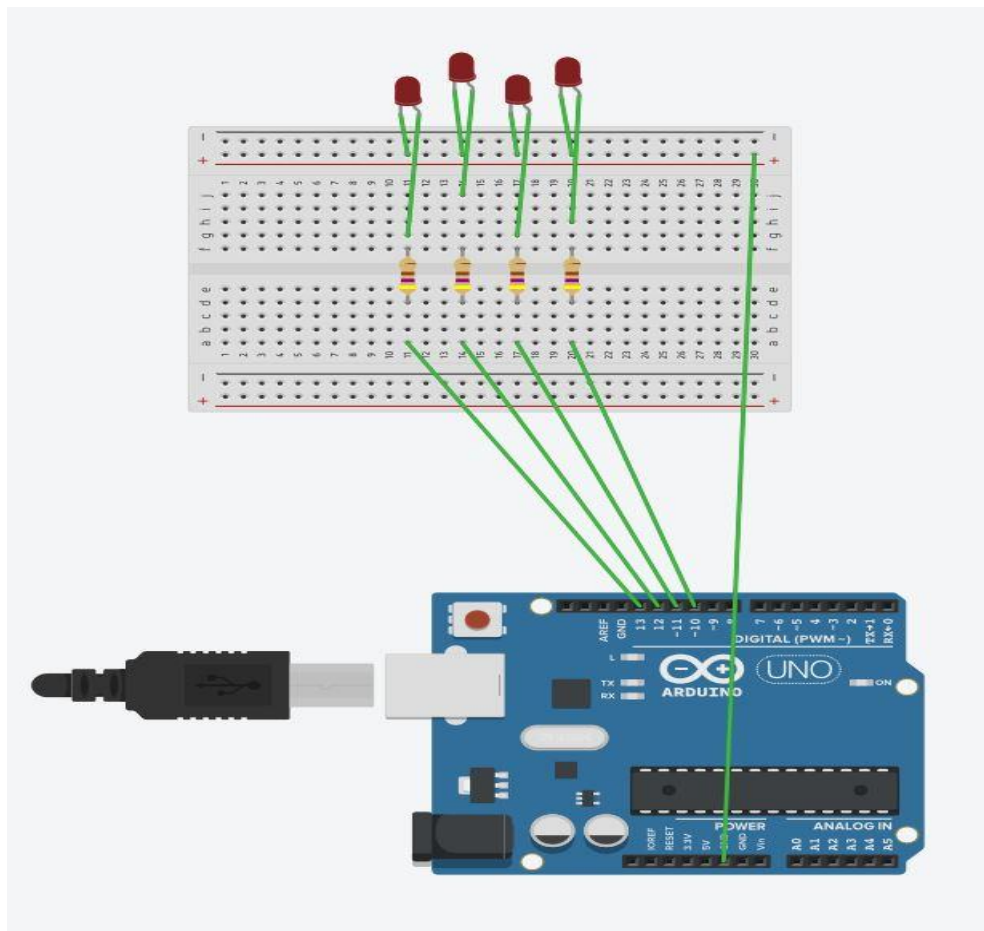


### **Circuit Diagram ->**



### **THEORY**

**Concepts Used ->** Arduino board, Breadboard and Multimeter, Diodes.

**Learning And Observations ->** Basic circuits of Arduino, Working of Diodes, Usages of Breadboard

**Problems and Troubleshooting ->** Diode should be connected in correct way, Resistance should be of appropriate magnitude, Wires should be properly connected.

**Precautions->** Diodes should be working, Resistance should be of appropriate magnitude, Pins on Arduino should be appropriately selected.

**Learning Outcomes->** We are now able to make basic Circuits using Arduino and have learnt the working of the diodes